

# Chapter 7 (Part I)

## Latches and Flip-Flops





# Latches

- Temporary storage device that has two stable states (bistable) or multivibrator.
- Be able to:
  1. Explain the operation of basic S-R latch
  2. Explain the operation of a gated S-R latch
  3. Explain the operation of a gated D latch
  4. Implement an S-R or D latch with logic gates

## S-R (Set-Reset) Latch

- Active-HIGH input S-R latch

  


$S$	$R$	$Q$	$\bar{Q}$	Remarks
0	0	NC	NC	No change
0	1	0	1	Latch RESET
1	0	1	0	Latch SET
1	1	?	?	Invalid Condition

Truth table for active-HIGH input S-R Latch




The active-HIGH S-R latch is in a stable (latched) condition when both inputs are LOW.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (0). To SET the latch ( $Q = 1$ ), a momentary HIGH signal is applied to the  $S$  input while the  $R$  remains LOW.

 To RESET the latch ( $Q = 0$ ), a momentary HIGH signal is applied to the  $R$  input while the  $S$  remains LOW.



   - Active-LOW input  $\bar{S}$  –  $\bar{R}$  latch



$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$	Remarks
0	0	?	?	Invalid Condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change (latch remain in present state, stable condition)


Truth table for active-LOW input  
 $\bar{S}$  –  $\bar{R}$  Latch

The active-LOW S-R latch is in a stable (latched) condition when both inputs are HIGH.

Assume the latch is initially RESET ( $Q = 0$ ) and the inputs are at their inactive level (1). To SET the latch ( $Q = 1$ ), a momentary LOW signal is applied to the  $\bar{S}$  input while the  $\bar{R}$  remains HIGH.

To RESET the latch a momentary LOW is applied to the  $\bar{R}$  input while  $\bar{S}$  is HIGH.

 
Never apply an active set and reset at the same time (invalid).




## Example

If the  $\bar{S} - \bar{R}$  waveforms are applied to the inputs of the latch. Determine the waveform that will be observed on the Q output. Assume that Q is initially LOW

## Solution

 

## Gated S-R (Set-Reset) Latch

 

- A gate input is added to the S-R latch to make the latch synchronous.
- The gated latch has an additional input, called enable ( $EN$ ) that must be HIGH in order for the latch to respond to the  $S$  and  $R$  inputs.
- When the enable input is LOW, the latch remains in the hold condition.




## Example

Determine the  $Q$  output waveform if the inputs shown below are applied to a gated S-R latch that is initially RESET
 
## Solution

Keep in mind that  $S$  and  $R$  are only active when  $EN$  is HIGH.



## Gated D Latch

 


Figure 7.9: Logic diagram for gated D Latch

 


Figure 7.10: Logic symbol for gated D Latch

$D$	$EN$	$Q$	$\bar{Q}$	Remarks
0	1	0	1	RESET
1	1	1	0	SET
X	0	NC	NC	No Change

Table 7.3: Truth table for gated D Latch


A simple rule for the *D* latch is:

*Q* follows *D* when the Enable is active.

## Example

Determine the *Q* output waveform if the inputs shown below are applied to a gated *D* latch that is initially RESET

## Solution

 

Notice that the Enable is not active during these times, so the output is latched.



# Flip-Flop


- Synchronous bistable devices aka bistable multivibrators.
- Be able to:
  1. Differentiate between latches and flip-flop
  2. Explain the operation of basic S-R, D and J-K flip-flop
  3. Explain flip-flop operating characteristic
  4. Discuss flip-flop applications


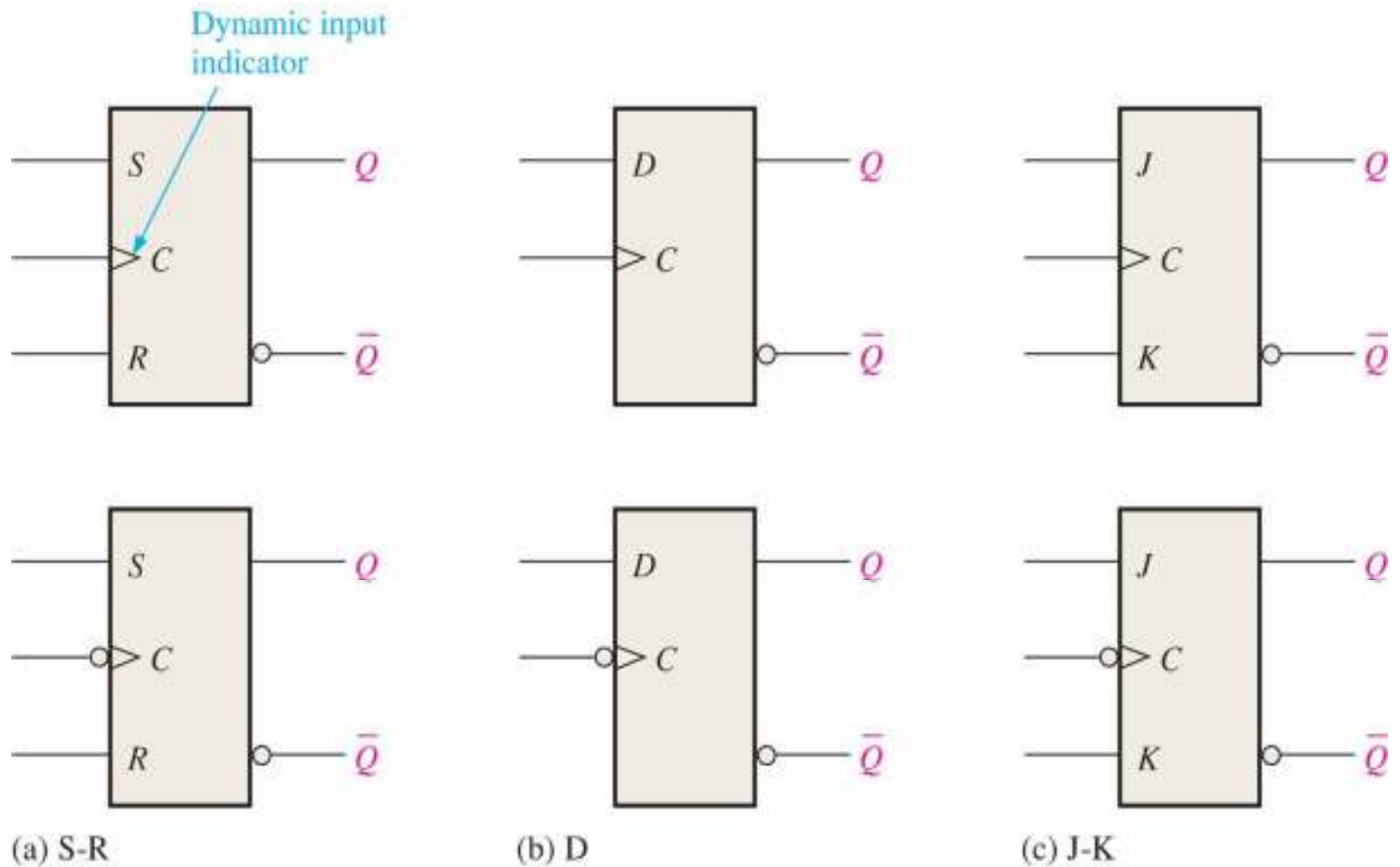
## Edge-Triggered flip-flop


- The output changes state only at a specified point on the triggering input called CLOCK (CLK), control input.
- Can be either positive edge triggered (no bubble at clock (C) input) or negative edge triggered (bubble at clock (C) input).

Edge-triggered flip-flop logic symbols (top: positive edge-triggered; bottom: negative edge-triggered).


 
# Clock Signal


- **Clock signal** is a **periodic square wave** that indefinitely **switches values** from 0 to 1 and 1 to 0 at **fixed intervals**.



Clock signal.
 
# Edge triggered S-R flip-flop

- **SET (S) and RESET (R) inputs** of the S-R flip-flop are called **synchronous input**.
- **Data** on these inputs are **transferred** to the output only **on the triggering edge** of the clock pulse.



Logic symbol for positive edge triggered S-R flip-flop

S	R	CLK	Q	$\bar{Q}$	Remarks
X	X	X	NC	NC	No Change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	?	?	Invalid Condition
↑ = clock transition from LOW to HIGH					
X = Don't care (0 or 1)					
NC = No change					
? = Invalid condition					


Truth table for positive edge triggered S-R flip-flop




## Example

Determine the  $Q$  and  $\bar{Q}$  output waveform of the positive edge triggered S-R flip-flop for the S, R and CLK input below. Assume that the flip-flop is initially RESET

## Solution

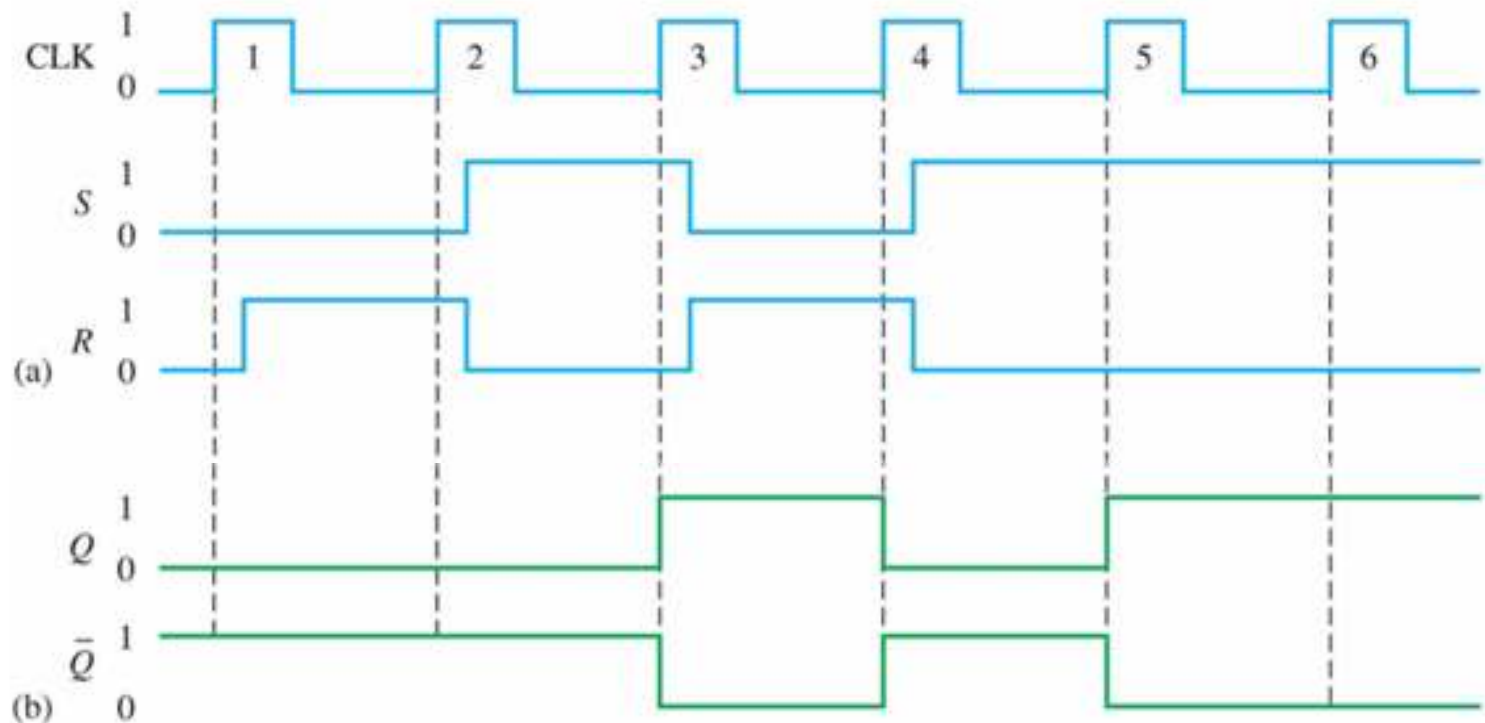


# Edge triggered D flip-flop

 

Logic symbol for positive edge triggered D flip-flop

D	CLK	Q		Remarks
X	X	NC	NC	No Change
1	↑	1	0	SET
0	↑	0	1	RESET
↑ = clock transition from LOW to HIGH				
X = Don't care (0 or 1)				
NC = No change				

 Truth table for positive edge triggered D flip-flop




A positive edge-triggered D flip-flop formed with an S-R flip-flop and an inverter

## Example


From the waveform for the D input and the clock, determine the Q output waveform if the flip-flop starts out RESET

## Solution

 
 
## Edge triggered J-K flip-flop

- Edge triggered J-K will **only accept** the  $J$  and  $K$  **inputs during** the **active edge** of the **clock**.



Logic symbol for positive edge triggered J-K flip-flop


$J$	$K$	$CLK$	$Q$	$\bar{Q}$	Remarks
X	X	X	$Q_0$	$\bar{Q}_0$	No Change
0	0	↑	$Q_0$	$\bar{Q}_0$	No Change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	$\bar{Q}_0$	$Q_0$	Toggle
↑ = clock transition from LOW to HIGH					
$Q_0$ = output level prior to clock transition					
X = Don't care (0 or 1)					

Truth table for positive edge triggered J-K flip-flop

## Example


From the waveform for the positive edge triggered J-K input and the clock, determine the Q output waveform if the flip-flop starts out RESET

## Solution

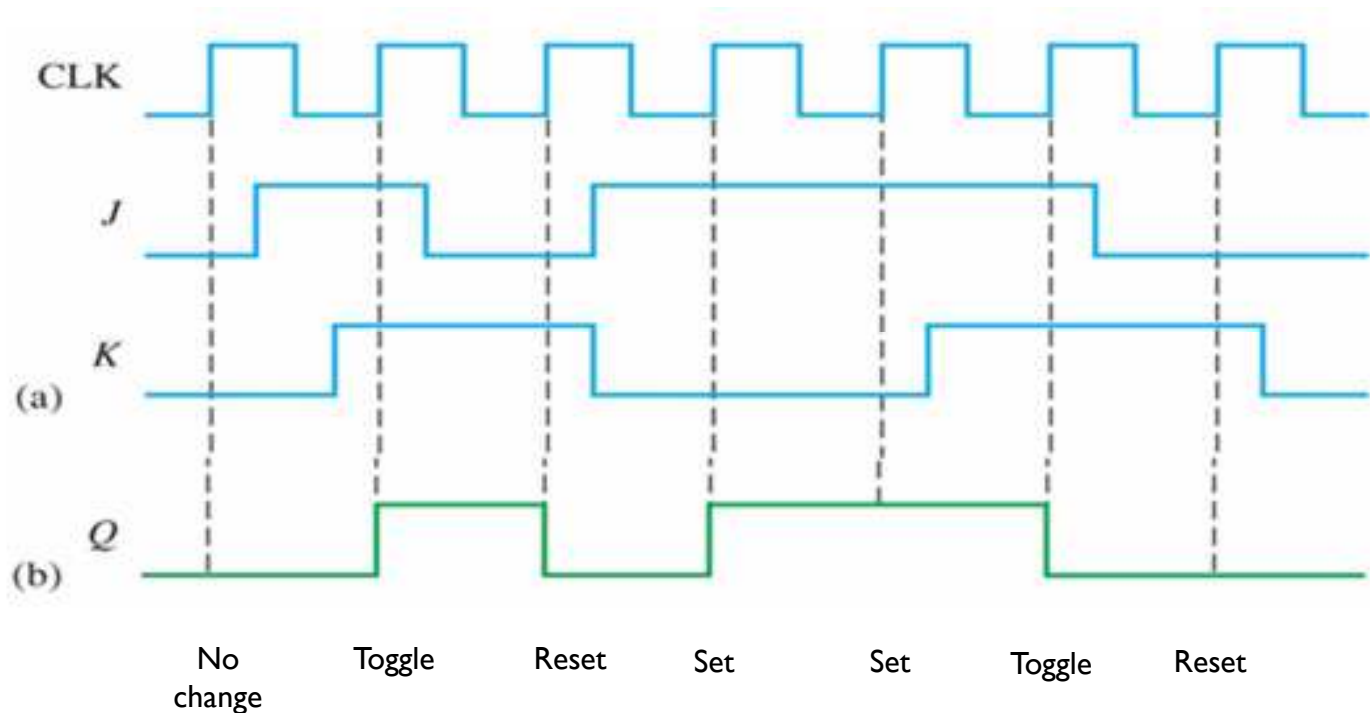

How about for negative edge triggered J-K flip flop?

# Asynchronous Preset and Clear Inputs


 


- Most flip-flops have other inputs that are *asynchronous*, meaning they affect the output independent of the clock.
- They are labeled as  $\overline{PRE}$  (preset) and  $\overline{CLR}$  (clear).
- An active level on preset input will set the flip-flop, and an active level on clear input will reset it.
- In normal condition, preset and clear would not be LOW at the same time. But must be kept HIGH for synchronous operation

## Example

Determine the Q output shown in the timing diagram if Q is initially LOW.


## Solution

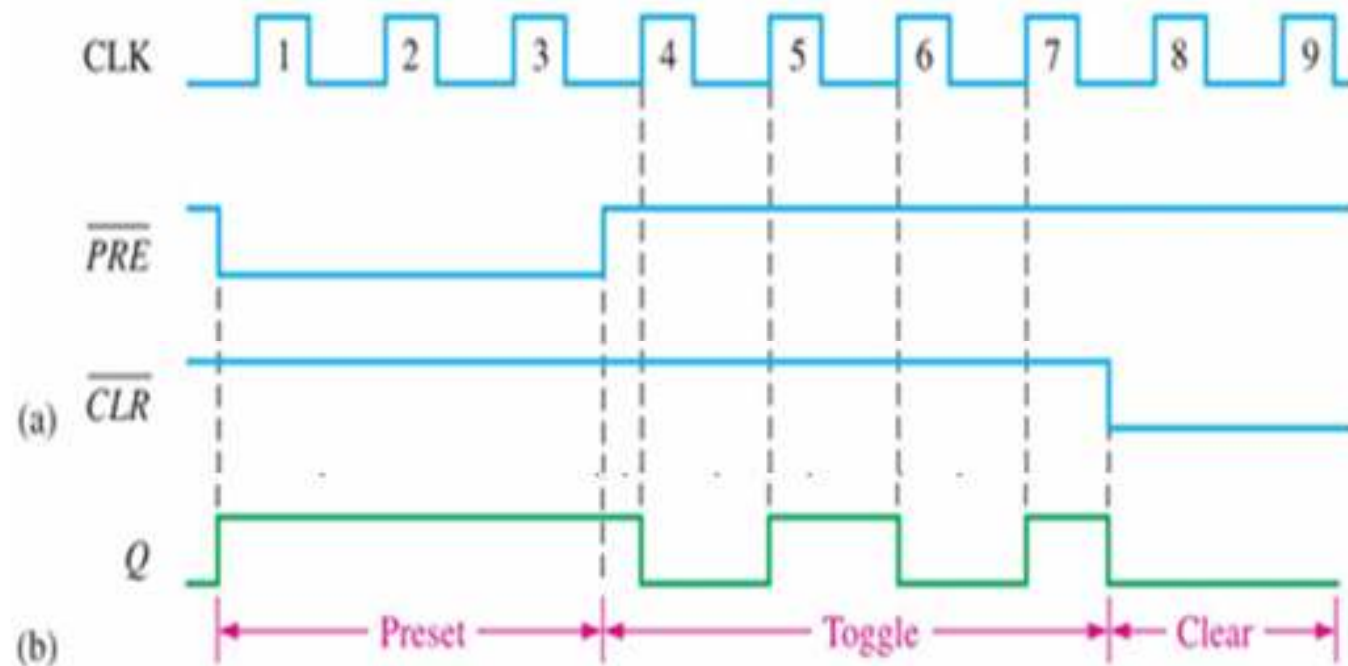 


 
# Flip-flop Operating Characteristic

**Propagation delay time** is specified for the rising and falling outputs. It is measured between the 50% level of the clock to the 50% level of the output transition.




The typical propagation delay time for the 74AHC family (CMOS) is 4 ns. Even faster logic is available for specialized applications.




**Set-up time** and **hold time** are times required before and after the clock transition that data must be present to be reliably clocked into the flip-flop.

 **Setup time** is the minimum time for the data to be present *before* the clock.



 **Hold time** is the minimum time for the data to *remain* after the clock.



**Maximum clock frequency**,  $f(\text{max})$ , highest rate at which a flip-flop can be reliably triggered. Above that the flip-flop will be unable to respond quickly.

# Assignment

- Examples of application of flip-flops are as follow:
  - Parallel Data Storage.
  - Frequency Division.
  - Counting.
- Discuss all the above applications by showing its logic circuit and timing diagram.
- Create a problem to show its application.
- Due date: 5<sup>th</sup> May 2014



# THE END OF PART III

LATCHES AND FLIP-FLOPS